
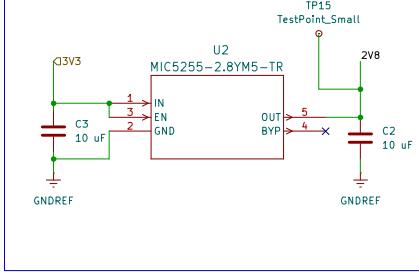


The buck regulator is efficient in stepping the voltage down from 15V to 3V3. The components around the regulator were taken from what the manufacturer suggested. The EN pin was said to be left floating for automatic startup.

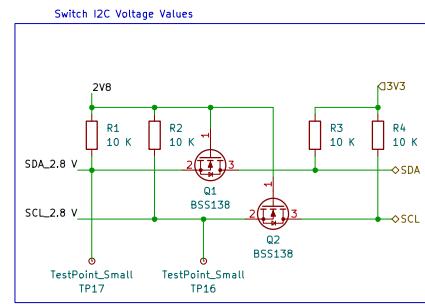
Sheet: /BuckRegulator/
File: Buckregulator.kicad_sch
Title: AirLift - HMS
Size: A4 **Date:** 12/02/2025
KiCad E.D.A. 9.0.6



Use of a linear regulator to step down the 3V3 to 2V8 since the distance sensor uses less voltage.




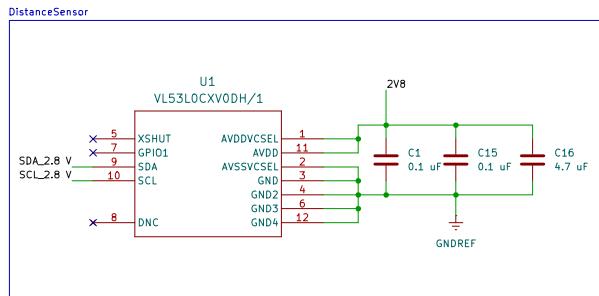Use of MOSFETS and resistors that change the 2V8 SDA and SCL lines from the distance sensor to 3V3 used by the ESP32. The change goes both ways since both are used for sending and receiving.



The distance sensor has only its SDA and SCL lines being used for the project. Uses 2V8 as input.

Sheet: /Distance/ File: Distance.kicad_sch		Cristian D. Garcia S.
Title: AirLift - HMS	Date: 12/02/2025	Rev: 4
Size: A4	KiCad E.D.A. 9.0.6	Id: 5/8

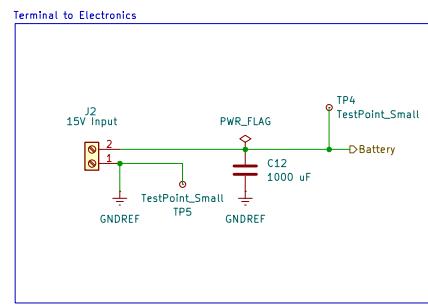

The terminal connects with a 15V battery. A big capacitor is used for stabilization of the current because of the MOSFETs constantly switching.

Sheet: /PSU/
File: PSU.kicad_sch

Title: Airlift - HMS


Size: A4 Date: 12/02/2025

KiCad E.D.A. 9.0.6


Cristian D. Garcia S.

Rev: 4

Id: 6/8

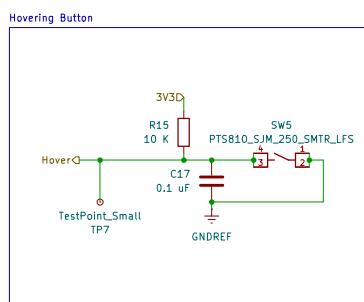

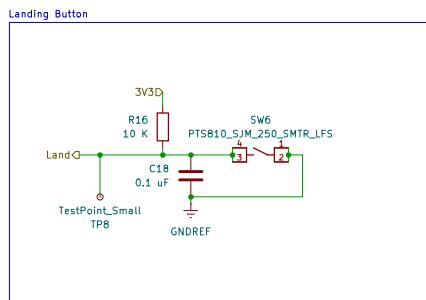Both buttons are normally HIGH and set to LOW when the buttons are pushed down. They are used as user input with protection for ESD.



Sheet: /Buttons/
File: Button.kicad_sch

Title: Airlift - HMS


Size: A4 Date: 12/02/2025


KiCad E.D.A. 9.0.6

Cristian D. Garcia S.

Rev: 4

Id: 7/8

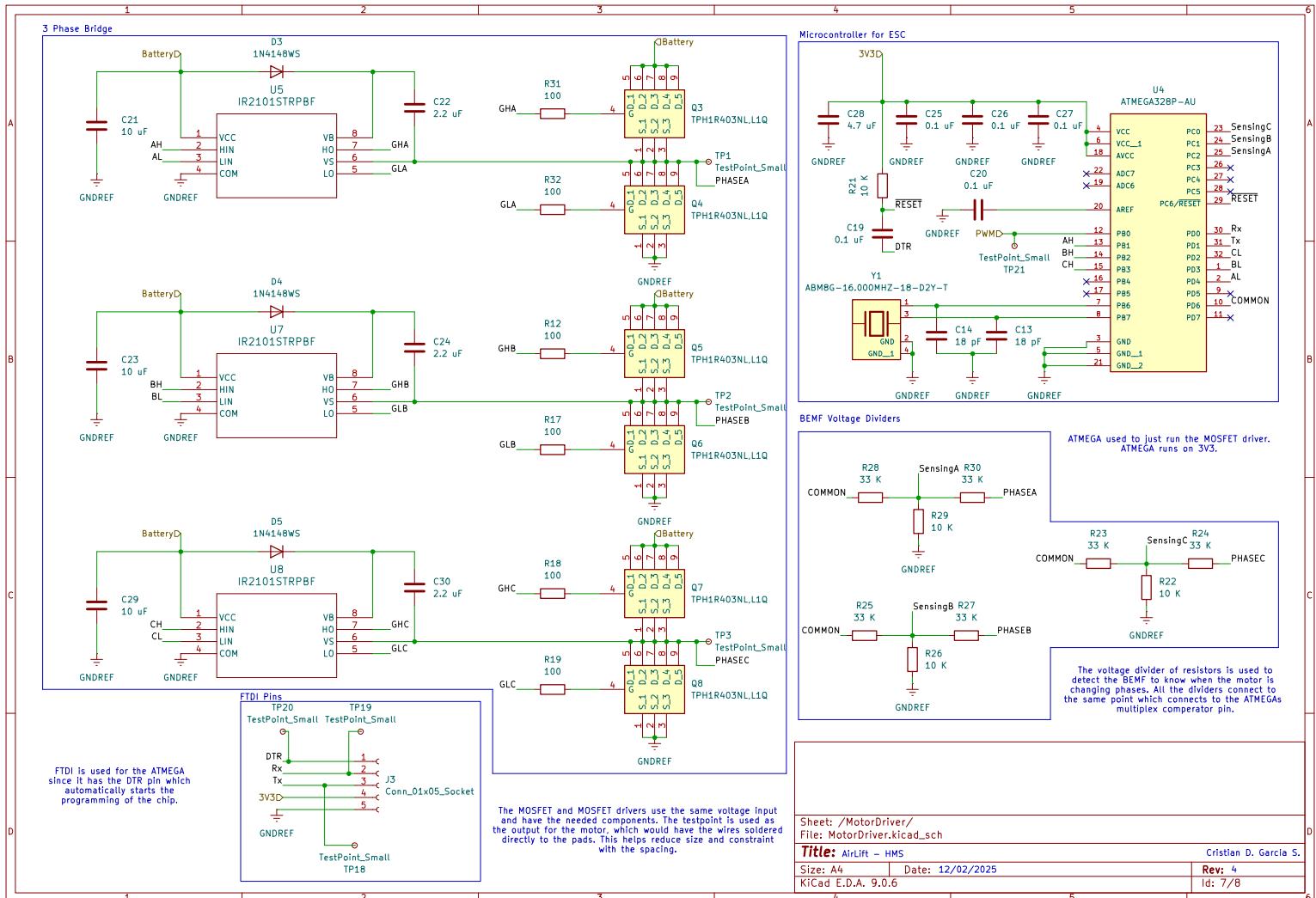

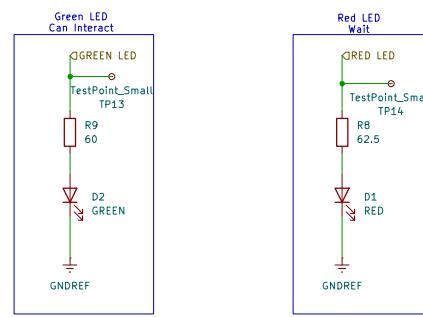

Use of two LEDs as user interface of the state of the drone.
The resistors have values so they have the same amount of current
going through both of them.

Sheet: /LED/
File: LED.kicad_sch

Title: Airlift - HMS

Size: A4	Date: 12/02/2025
KiCad E.D.A. 9.0.6	

Cristian D. Garcia S.

Rev: 4
Id: 9/8